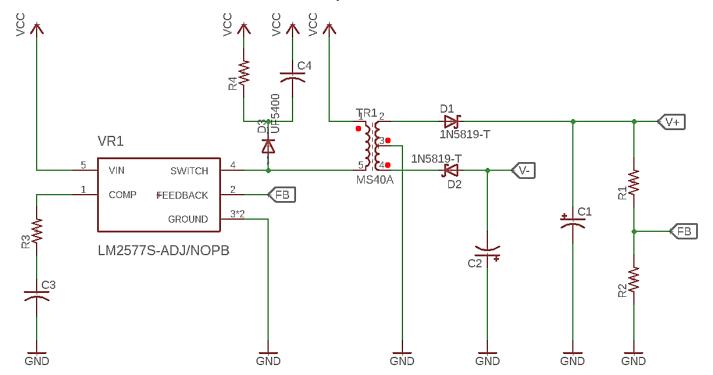


# Fuente flyback



Relación de transformación:

$$\frac{V_p}{V_s} = \frac{n_1}{n_2} \cong \frac{I_2}{I_1} \quad [1]$$


Relación de impedancias:

$$\frac{Z_1}{Z_2} = \frac{n_1^2}{n_2^2} \quad [2]$$


Conocido  $A_L$  podemos despejar el número de espiras o sabiendo el número de espiras y la inductancia calculamos  $A_L$ :
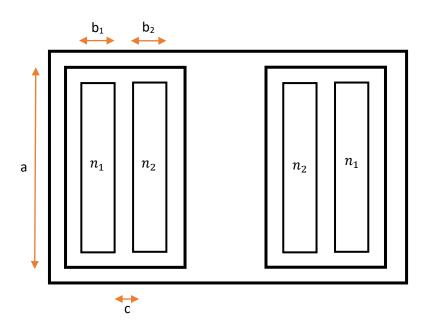
$$n = \sqrt{\frac{L}{A_L}} \quad \text{o} \quad A_L = \frac{L}{n^2}$$




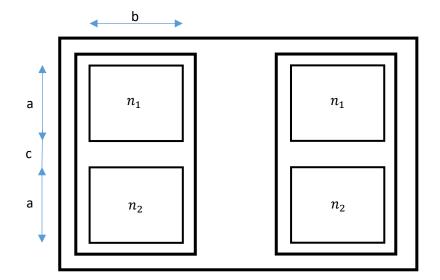
$$L_{d1} = \frac{1.2 l_m n_1^2}{a} \left( c + \frac{b_1 + b_2}{3} \right) 10^{-10}$$



$$L_{d2} = \frac{1.33 \ l_m \ n_1^2}{b} \left( c + \frac{\sum a}{3} \right) 10^{-10}$$



### Procedimiento de diseño

#### 1. Selección del transformador

Transformer Type		Input Voltage	Dual Output	Maximum Output
	L <sub>P</sub> = 100 μH	5V	±10V	325 mA
1	N = 1	5V	±12V	275 mA
		5V	±15V	225 mA
		10V	±10V	700 mA
		10V	±12V	575 mA
2	L <sub>P</sub> = 200 μH	10V	±15V	500 mA
	N = 0.5	12V	±10V	800 mA
		12V	±12V	700 mA
		12V	±15V	575 mA
3	L <sub>P</sub> = 250 μH	15V	±10V	900 mA
	N = 0.5	15V	±12V	825 mA
		15V	±15V	700 mA

#### 2. Red de compensación

$$R_c \le \frac{750 \, I_{Max} \, \left(15 + V_{in(min)} \, N\right)^2}{V_{in(min)}^2}$$


Donde  $I_{Max}$  es la corriente máxima requerida en ambas salidas.

$$C_{out} \ge \frac{0.19 R_c L_p I_{Max}}{15 V_{in(min)}}$$

$$C_C \ge \frac{58.5 \ C_{out} \ V_{out} \ \left(V_{out} + \left(V_{in(min)} \ N\right)\right)}{R_c^2 \ V_{in(min)} \ N}$$
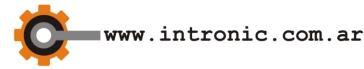
## 3. Fórmulas del regulador Flyback

$$D = \frac{V_{out} + V_F}{N(V_{in} - V_{sat}) + V_{out} + V_F}$$





$$\Delta I_p = \frac{D(V_{in} - V_{sat})}{L_p 52000}$$

$$I_{p(PK)} = \frac{N}{\eta} \frac{I_{Max}}{1 - D} + \frac{\Delta I_p}{2}$$

$$V_{Sw(off)} = V_{in} + \frac{V_{out} + V_F}{N}$$

$$V_{out} = 1.23 \left( 1 + \frac{R_1}{R_2} \right)$$

# 4. Red snubber

$$C \ge \frac{0.02 L_p I_{p(PK)}^2}{\left(V_{clamp}^2 - V_{Sw(off)}\right)^2}$$

$$R \le \left(\frac{V_{clamp} + V_{Sw(off)} - V_{in}}{2}\right)^2 \left(\frac{19.2 \ 10^{-4}}{L_p \ I_{p(PK)}^2}\right)$$

